

Ex. No. 13	CIRCUIT ANALYSIS WITH DEPENDENT SOURCES
Date:	

AIM:

1. To model dependent voltage sources and current sources in LT Spice
2. To find the nodal voltages and branch currents



SIMULATION SOFTWARE:

LT Spice – DC operating point analysis and transient analysis.

CIRCUITS:



Voltage Controlled Voltage Source (VCVS):

- Find V_x

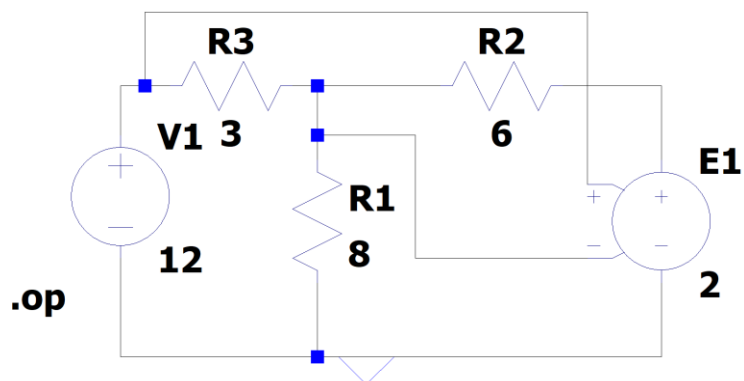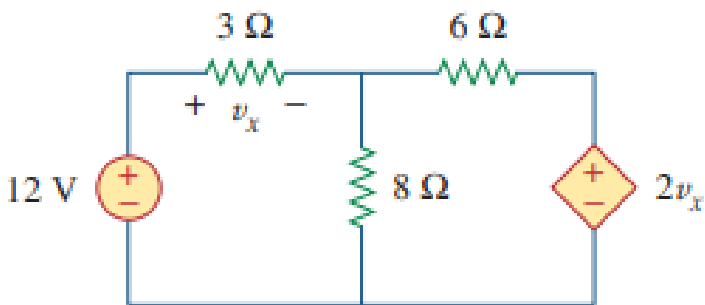


Voltage Controlled Current Source (VCCS):


- Find V_x

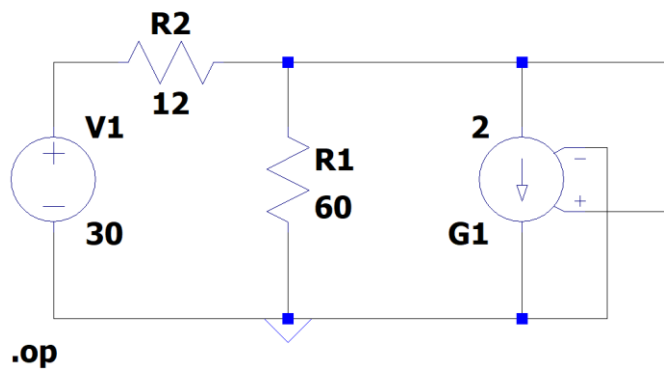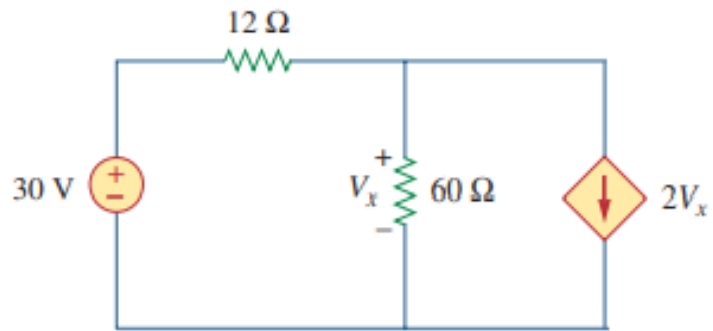

Current Controlled Voltage source (CCVS):



- Find i

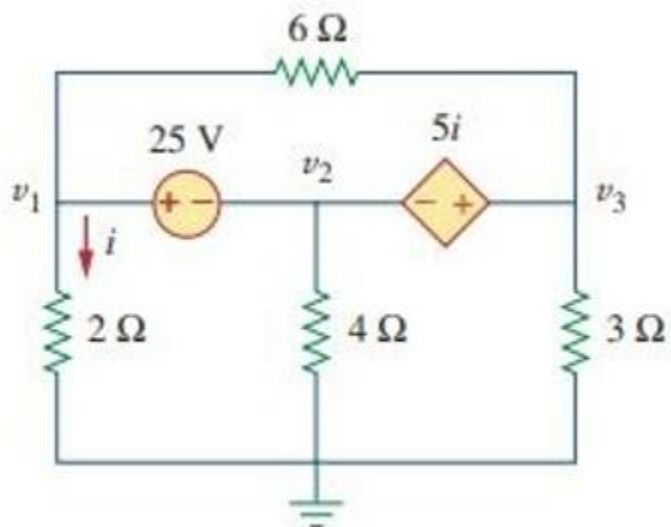

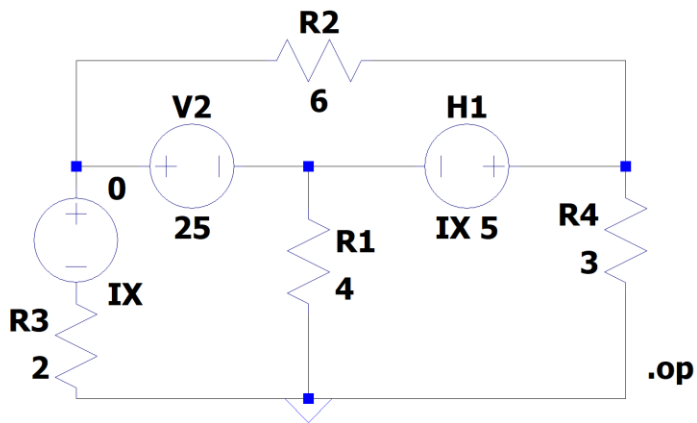

Current Controlled Current Source (CCCS):

- Find V_o and I_x

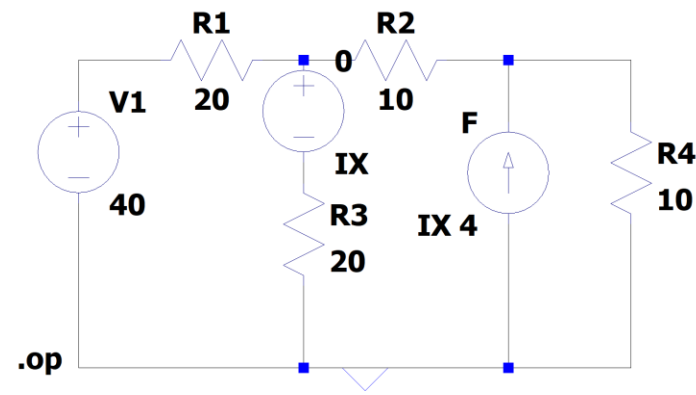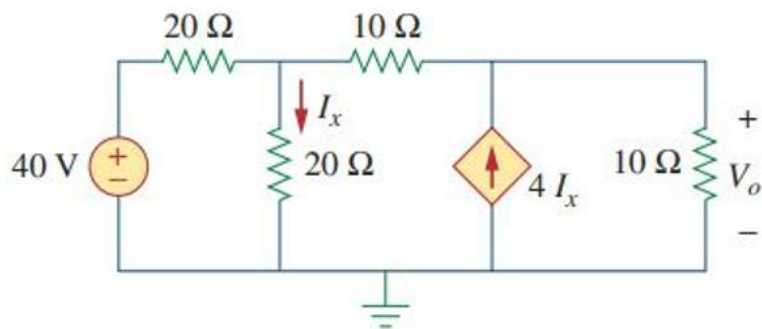


Hand Calculations:

Simulations Results:

Inference:

Results:

Current Controlled Current Source (CCCS)

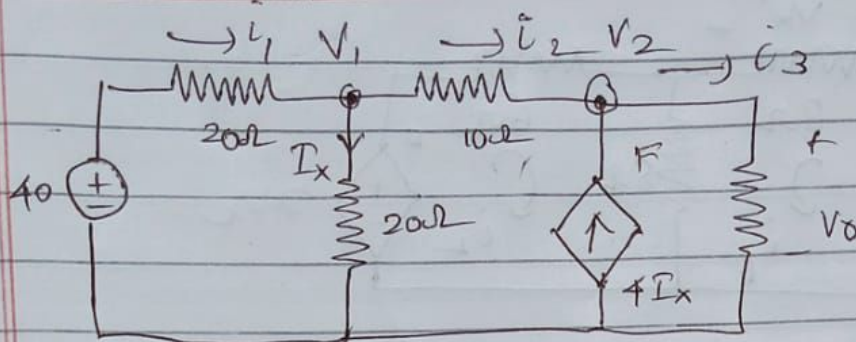

$$i_1 = I_x + i_2$$

$$\frac{40 - V_1}{20} = \frac{V_1}{20} + \frac{V_1 - V_2}{10}$$

$$40 = 4V_1 - 2V_2 \quad (1)$$

$$i_2 + 4I_x = i_3$$

$$\frac{V_1 - V_2}{10} + 4 \frac{V_1}{20} = \frac{V_2}{10} \quad (2)$$

$$3V_1 = 2V_2$$

$$I_x = \frac{V_1}{20}$$

$$V_0 = V_2$$


$$\therefore V_1 = 40V$$

$$V_2 = 60V$$

$$\therefore I_x = 2A$$

$$V_0 = 60V$$

Voltage Controlled Current Source (VCCS)

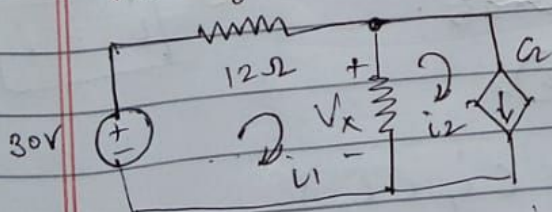

$$i_2 = 2V_x = 2(60i_1 - i_2)$$

$$\therefore V_x = 60(i_1 - i_2) = 120i_1 - 120i_2$$

at mesh ① $30 = 12i_1 + 60(i_1 - i_2)$


Solution

$$i_2 = 2.38A$$

$$i_1 = 2.4A$$

$$V_x = 60(i_1 - i_2) = 1.2V$$

Voltage Dependent Voltage Source (VCVS)

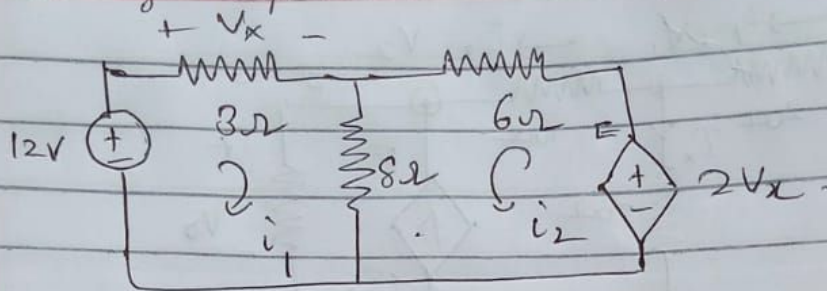

$$3i_1 + 8(i_1 + i_2) = 12$$

$$2V_x = 6i_2 + 8(i_1 + i_2)$$


$$V_x = 3i_1$$

$$i_2 = -0.1739 \text{ A}$$

$$i_1 = 1.2739 \text{ A}$$

$$V_x = 3.625 \text{ V}$$

Current Controlled Voltage Source (CCVS)

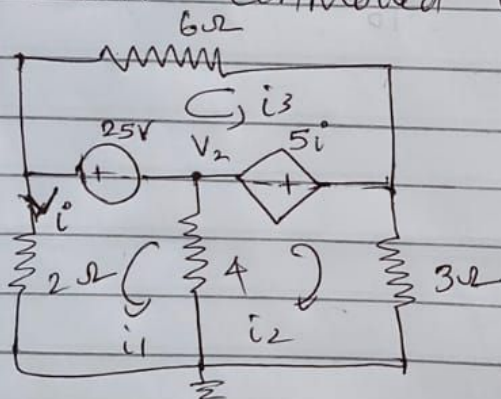

KVL around Mesh ①.

$$-25 + 2i_1 + 4(i_1 + i_2) = 0$$

$$6i_1 + 4i_2 = 25$$

$$\boxed{i_1 = i}$$

KVL around Mesh ②.

$$5i = 3i_2 + 4(i_1 + i_2)$$

$$3i_2 + 4i_1 + 4i_2 = 5i$$

$$4i_1 + 7i_2 = 5i \quad \text{but } i = i_1$$

$$-1i_1 + 7i_2 = 0 \quad \text{②}$$

KVL around Mesh (3)

$$6i_3 + 25 - 5i_1 = 0$$

$$6i_3 - 5i_1 = -25 \quad (3)$$

$$-5i_1 + 6i_3 = -25 \quad (3)$$

$$6 \quad 4 \quad 0 \quad 25$$

$$-1 \quad 7 \quad 0 \quad 0$$

$$-5 \quad 0 \quad 6 \quad -25$$

$$i_1 = 3.8$$

$$i_2 = 0.54$$

$$i_3 = -0.996$$

$$\text{Current controlled voltage source} = 5 \times i_1$$

$$= 5 \times 3.8$$

$$= 19V$$